
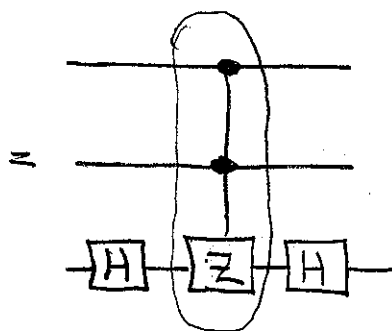


Solution


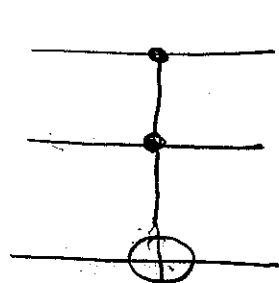
1.5. Constructing a circuit for the Toffoli gate



We'll construct $C^{(2)}(Z)$

$$\text{Let } U_\theta \equiv e^{i\theta/2} U_Z(\theta) = e^{i\theta/2} e^{-iZ\theta/2} \leftrightarrow \begin{pmatrix} 1 & 0 \\ 0 & e^{i\theta} \end{pmatrix}$$

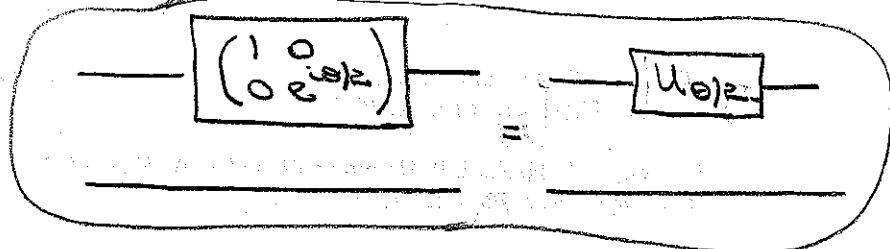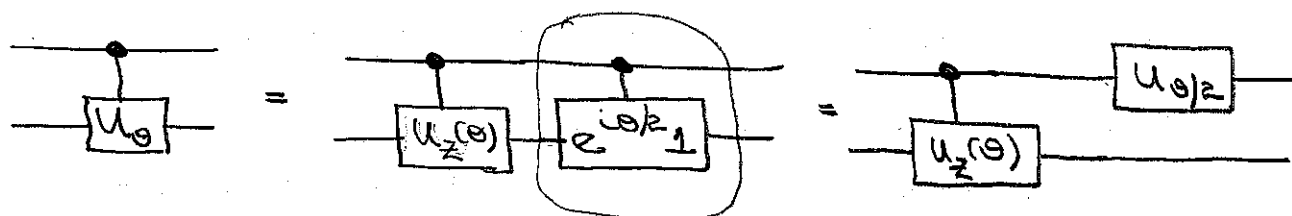(a) First construct $C^{(1)}(U_\theta) =$



$$\text{Write } U_Z(\theta) = U_Z^2(\theta/2)$$

$$X U_Z(\alpha) X = X e^{-iZ\alpha/2} X = e^{iZ\alpha/2} = U_Z^\dagger(\alpha)$$


$$\uparrow \\ XZX = -Z$$

$$U_Z(\alpha) = X U_Z^\dagger(\alpha) X$$


This is the basic fact we're going to live on.

$$U_z(\theta) = U_z(\theta/2) \times U_z^\dagger(\theta/2) \times = \times U_z^\dagger(\theta/2) \times U_z(\theta/2) \\ = U_{\theta/2} \times U_{\theta/2}^\dagger \times = \times U_{\theta/2}^\dagger \times U_{\theta/2}$$

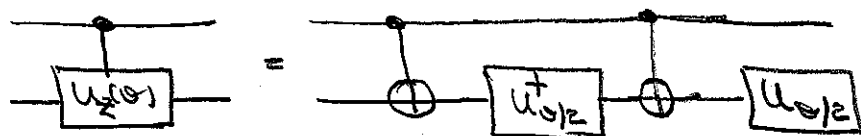
These are the decompositions of NC Corollary 4.2, simpler here because we're dealing with rotations about the z axis.



Putting things together, we get

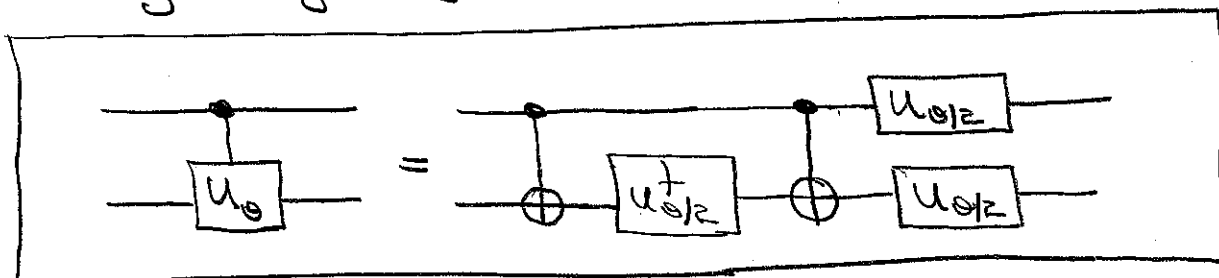

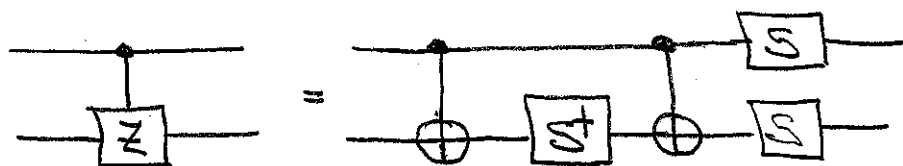
$$\theta = \pi: U_\pi = Z, U_{\pi/2} = S$$




Kind of an odd decomposition for C-SIGN, but it does work.

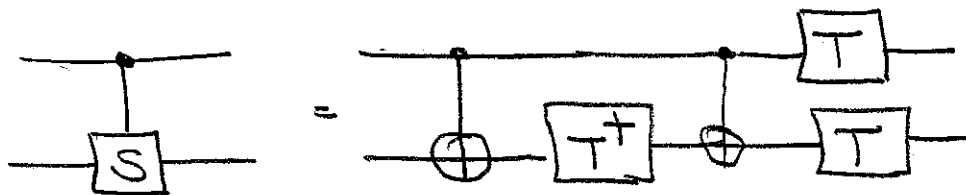
$$\theta = \pi/2: U_{\pi/2} = Z, U_{\pi/4} = T$$




We have

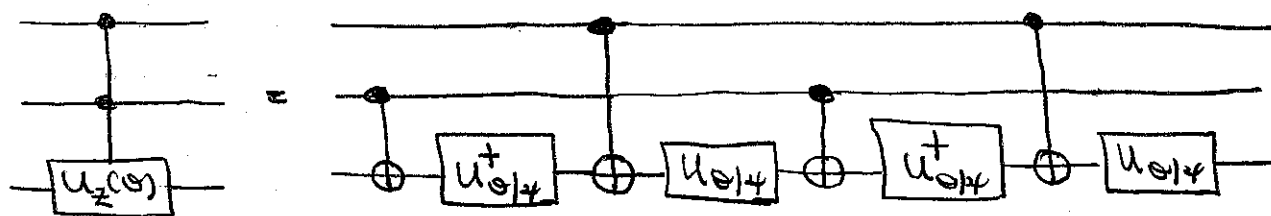

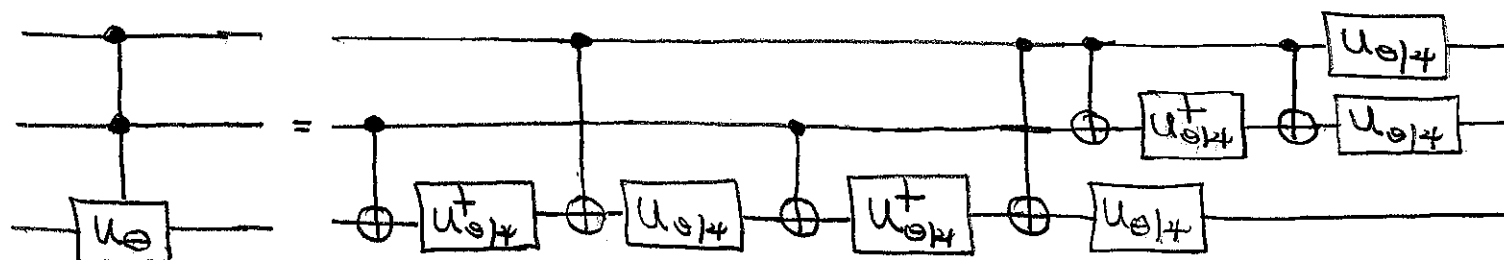Expanding the circuit at the top of p. 3, we get



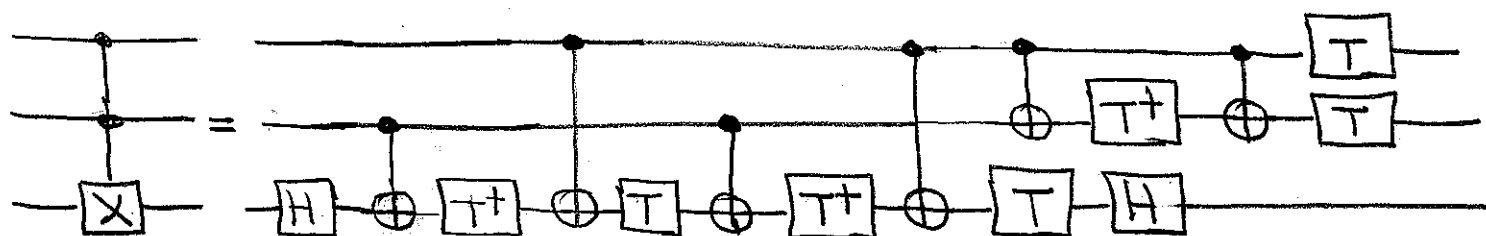$\theta = \pi$ gives $C^{(2)}(Z)$, with $U_{\pi/4} = T$. By including Hadamards at the beginning and end of the target wire, we get the Toffoli, $C^{(2)}(X)$.



This circuit differs from NC's Figure 4.9 by the final gates on the control wires. These final gates are a controlled- S , which is necessary to adjust relative phases. The textbook uses a different circuit for the controlled- S .