

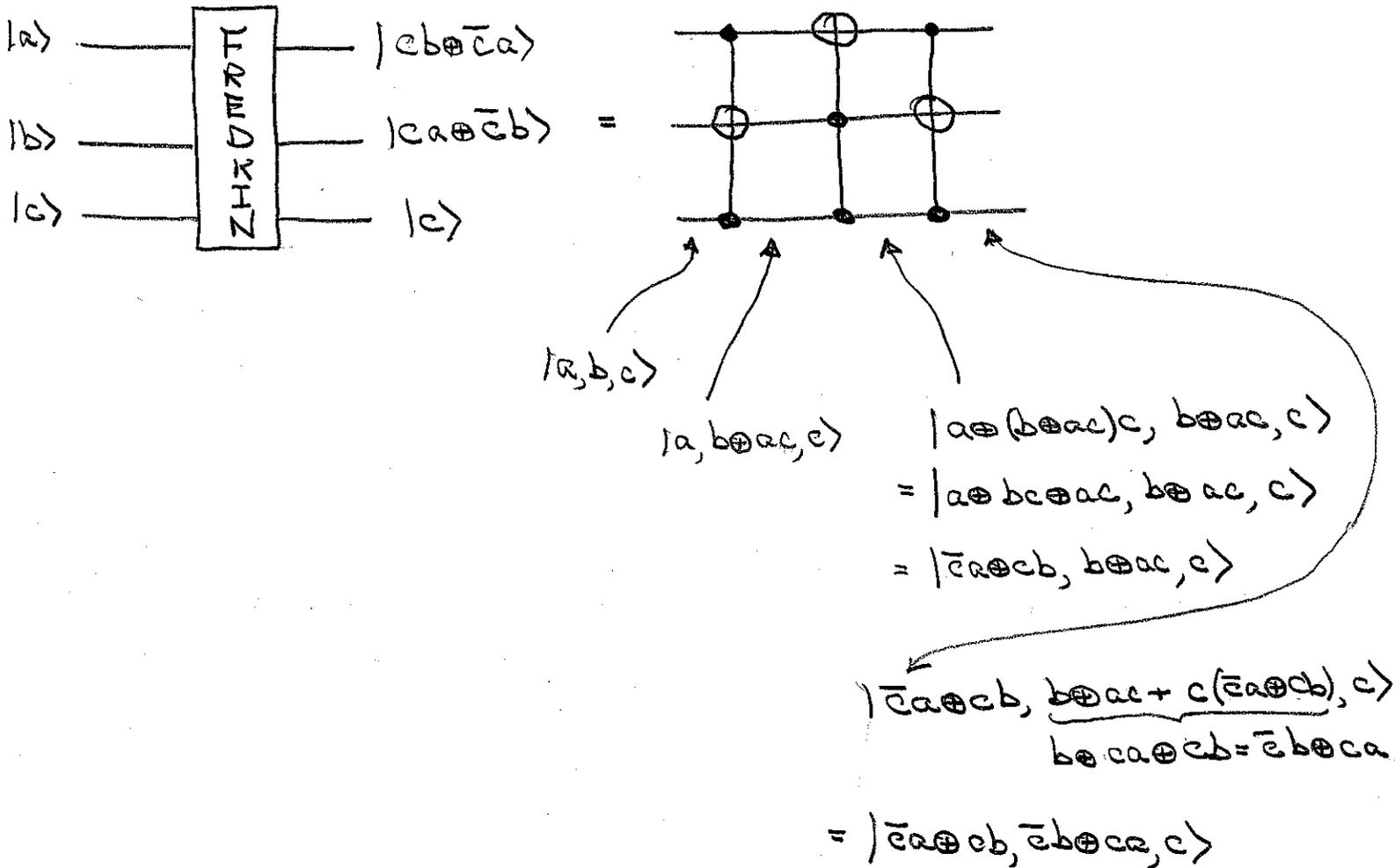


Solution 1.6.


SWAP

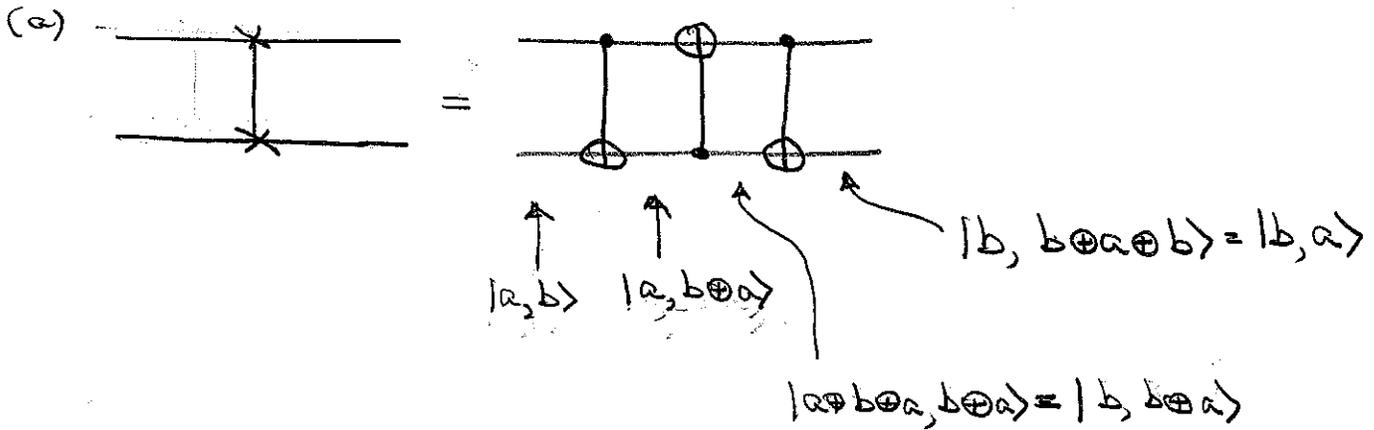

Circuit for 2-level transition $|000\rangle \rightarrow |111\rangle$
 $|111\rangle \rightarrow |000\rangle$

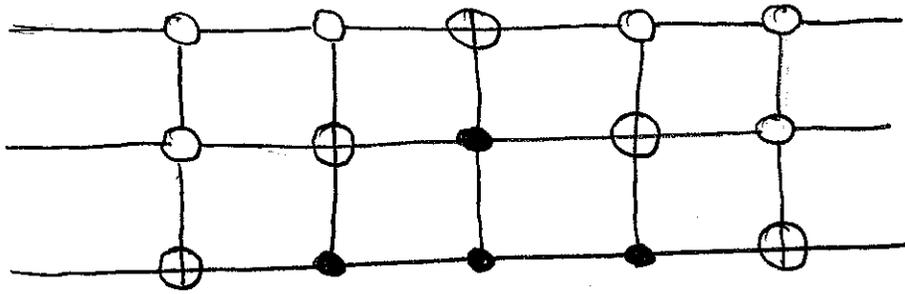

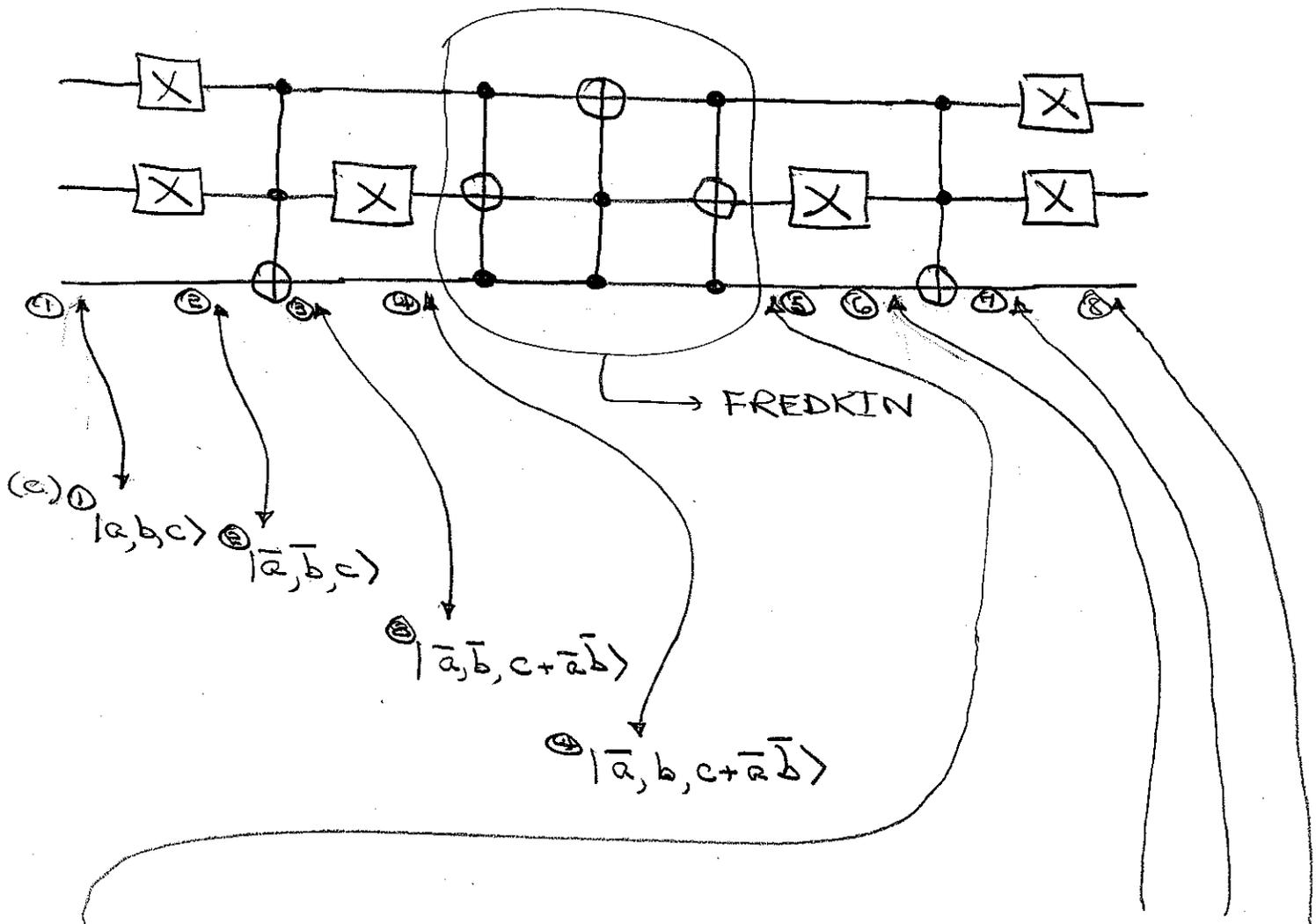(b) We convert a control-on-0 to a control-on-1 by putting an X gate on each side of the control. On the top line all these X's annihilate except the outer two, so the circuit becomes



$$\downarrow$$

$$|(c + \bar{a}\bar{b})b + (\bar{c} + \bar{a}\bar{b})\bar{a}, (c + \bar{a}\bar{b})\bar{a} + (\bar{c} + \bar{a}\bar{b})b, c + \bar{a}\bar{b}|$$

$bc + \bar{a}\bar{c} + \bar{a}\bar{b}$	$\bar{a}c + \bar{a}\bar{b} + b\bar{c}$	$c + 1 + a + b + ab$
$= bc + \cancel{x} + \cancel{y} + c + ac$	$= c + ac + 1 + a + \cancel{b} + ab$	$= 1 + a + b + c + ab$
$+ \cancel{x} + \cancel{y} + b + ab$	$+ \cancel{b} + bc$	
$= b + c + g$	$= 1 + a + c + g$	

$$\textcircled{5} = |b + c + g, 1 + a + c + g, 1 + a + b + c + ab|$$

$$\textcircled{6} |b + c + g, a + c + g, 1 + a + b + c + ab|$$

$$|b + c + g, a + c + g, 1 + a + b + c + ab + \underbrace{(b + c + g)(a + c + g)}_{(c + g)(b + c) + (a + b)g + g}|$$

$$= c + g + (a + b)g + g$$

$$= c + (a + b)g$$

$$= c + \cancel{ab} + \cancel{ac} + \cancel{bc} + \cancel{cb} + \cancel{bc} + \cancel{cb}$$

$$= c + ac + bc$$

$$1 + a + b + g = a + b + \bar{g}$$

$$\textcircled{7} = |b + c + g, a + c + g, a + b + \bar{g}|$$

$$\textcircled{8} |b \oplus c \oplus \bar{g}, a \oplus c \oplus \bar{g}, a \oplus b \oplus \bar{g}|$$

It is easy to verify that the 3-bit function

$$\begin{pmatrix} a \\ b \\ c \end{pmatrix} \rightarrow \begin{pmatrix} b \oplus c \oplus 1 \\ a \oplus c \oplus 1 \\ a \oplus b \oplus 1 \end{pmatrix}$$

exchanges 000 and 111 and leaves all other inputs unchanged.