

Quantum computation

Lecture 1

Classical circuit model

Classical computational models

- ① Turing machine ← we're not going to discuss
- ② Circuit model: bits, wires, gates

Single-bit gates

IDENTITY $a \rightarrow a$

a	a
0	0
1	1


NOT $a \rightarrow \text{NOT} \rightarrow \bar{a} = 1 \oplus a$

a	$\bar{a}$
0	1
1	0

FANOUT (COPY)


CROSSOVER (SWAP)

AND

 

a	b	ab
0	0	0
0	1	0
1	0	0
1	1	1

OR

 

a	b	$a \oplus b \oplus ab$
0	0	0
0	1	1
1	0	1
1	1	1


XOR



a	b	$a \oplus b$
0	0	0
0	1	1
1	0	1
1	1	0

← No nonlinear piece

NAND

 


a	b	$1 \oplus ab$
0	0	1
0	1	1
1	0	1
1	1	0

Two-bit gates

2 inputs

NOR

 

a	b	$\bar{a}\bar{b}$
0	0	1
0	1	0
1	0	0
1	1	0

Only 2-bit gates (quadratic and linear polynomials) required.

We could go on, but these are enough to do anything. What is it we want to do?



Evaluate functions $f: \{0,1\}^N \rightarrow \{0,1\}^M$ that map N bits to M bits. But $M=1$ is good enough: Boolean functions (decision problems).

There are 2^{2^N} Boolean functions on N bits. The single- and two-bit gates are $N=1$ and $N=2$ Boolean functions.

Factoring
 $f(x,y) = \begin{cases} 1 & \text{if } x \text{ has factor } y \\ 0 & \text{otherwise} \end{cases}$


Example: adding $x = x_2x_1x_0$ and $y = y_2y_1y_0$

x	y	c	$x \oplus y$
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

  

Binary version of the add-and-carry method taught to school children

x	y	c	c'	$x \oplus y \oplus c$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 

Computing any Boolean function:

$N=1$: 4 functions

IDENTITY

a	a
0	0
1	1



NOT


a	$\bar{a}$
0	1
1	0



a	0
0	0
1	0



a	1
0	1
1	1

 

Need
NOT, AND,
and OR +
ancilla bits

Induction: Assume there is a circuit for any Boolean function on N bits

f an $(N+1)$ -bit function

f_0 and f_1 N -bit functions defined by


$$f_0(x_1, \dots, x_N) \equiv f(0, x_1, \dots, x_N)$$

$$f_1(x_1, \dots, x_N) \equiv f(1, x_1, \dots, x_N)$$

$$f_{x_0}(x_1, \dots, x_N) \equiv f(x_0, x_1, \dots, x_N)$$


i.e., $f_{x_0}(x_1, \dots, x_N) \equiv f_0(x_1, \dots, x_N) \oplus x_0 f_1(x_1, \dots, x_N)$
 
$$f(x_0, x_1, \dots, x_N) = (1 \oplus x_0) f_0(x_1, \dots, x_N) \oplus x_0 f_1(x_1, \dots, x_N)$$




We can evaluate any Boolean function using


wires and ancilla bits

 

 
If we can use ancilla bits and FANOUT, we can get all these from NAND




AND

 


OR

 

XOR

 

 So with ancilla bits, and FANOUT, NAND is a universal gate.



Computational complexity

Σ gates

$$\sum \begin{pmatrix} x \\ y \end{pmatrix} + \sum \begin{pmatrix} x \\ y \end{pmatrix} = \sum \begin{pmatrix} x \\ y \end{pmatrix}$$

$$\sum \begin{pmatrix} x \\ y \end{pmatrix} = \sum \begin{pmatrix} x \\ y \end{pmatrix}$$

General 2-bit gates: $\begin{pmatrix} x' \\ y' \end{pmatrix} = M \begin{pmatrix} x \\ y \end{pmatrix} \oplus \begin{pmatrix} a \\ b \end{pmatrix}$

Reversible classical computation.

Why?

Energy dissipation

Quantum computation is inherently reversible.

Any irreversible function $f: \{0,1\}^N \rightarrow \{0,1\}^M$ can be imbedded in a function $\tilde{f}: \{0,1\}^{N+M} \rightarrow \{0,1\}^{N+M}$ such that

$$\tilde{f} \left(\begin{matrix} x \\ 0^M \end{matrix} \right) = (x, f(x)).$$

$\tilde{f}$ can be extended to a 1-1 function, e.g.,

$$\tilde{f}(x, y) = (x, y \oplus f(x))$$

not a unique extension, but we will generally use it as the reversible function.

But can we do this with reversible gates?

N_{in}, N_{out}

N -bit gates

$N=1$

$N=2$

4

256


$(2^N)!$ N -bit reversible gates

2

24

permutations of the 2^N input strings

 CNOT is an example: XOR placed in 2nd bit, with first bit unchanged



Can get CROSSOVER from 3 CNOT's.

The 2 -bit reversible gates are all

linear, with invertible M ; they do not have the irreversible, nonlinear xy piece.

$$\begin{pmatrix} x \\ y \end{pmatrix} \rightarrow \begin{pmatrix} x' \\ y' \end{pmatrix} = M \begin{pmatrix} x \\ y \end{pmatrix} \oplus \begin{pmatrix} a \\ b \end{pmatrix}$$


$$M = \begin{pmatrix} 1 & 0 \\ 0 & 1 \end{pmatrix}, \begin{pmatrix} 0 & 1 \\ 1 & 0 \end{pmatrix}, \begin{pmatrix} 1 & 1 \\ 0 & 1 \end{pmatrix}, \begin{pmatrix} 1 & 0 \\ 1 & 1 \end{pmatrix}, \begin{pmatrix} 0 & 1 \\ 1 & 1 \end{pmatrix}, \begin{pmatrix} 1 & 1 \\ 1 & 0 \end{pmatrix}$$

$$\begin{pmatrix} a \\ b \end{pmatrix} = \begin{pmatrix} 0 \\ 0 \end{pmatrix}, \begin{pmatrix} 1 \\ 0 \end{pmatrix}, \begin{pmatrix} 0 \\ 1 \end{pmatrix}, \begin{pmatrix} 1 \\ 1 \end{pmatrix}$$

24 reversible 2-bit gates

We need 3-bit reversible gates to get a universal set.

Fredkin gate:

 


a	b	c	a'	b'	c'
0	0	0	0	0	0
0	0	1	0	0	1
0	1	0	0	1	0
0	1	1	1	0	1
1	0	0	1	0	0
1	0	1	0	1	1
1	1	0	1	1	0
1	1	1	1	1	1

$c=0: (a,b) \rightarrow (a,b)$


$c=1: (a,b) \rightarrow (b,a)$

controlled swap (crossover)


FREDKIN is its own inverse.

 

CROSSOVER

 

AND

 


NOT

FANOUT


NOT and AND give NAND,
so FREDKIN is a universal gate

Toffoli gate: CCNOT

 


a	b	c	a	b	$c \oplus ab$
0	0	0	0	0	0
0	0	1	0	0	1
0	1	0	0	1	0
0	1	1	0	1	1
1	0	0	1	0	0
1	0	1	1	0	1
1	1	0	1	1	1
1	1	1	1	1	0


TOFFOLI is its own inverse.

 

 TOFFOLI is a universal gate. (if you know it)



Complexity?

 

Complexity?