

Homework Problem 2.1
(10 points)

Due Thursday, September 24
(at lecture)

2.1 Transformation of Pauli products by C-NOT and C-SIGN. Let C denote either the controlled-NOT gate or the controlled-SIGN gate, with the first qubit as control and the second qubit as target. In this problem we investigate how C-NOT and C-SIGN transform Pauli products.

(a) Use circuit identities to derive the following transformations for $C = \text{C-NOT}$:

$$C(X \otimes I)C^\dagger = X \otimes X$$

$$C(I \otimes X)C^\dagger = I \otimes X$$

$$C(Z \otimes I)C^\dagger = Z \otimes I$$


$$C(I \otimes Z)C^\dagger = Z \otimes Z .$$

(b) Use the transformations of part (a) to derive how the C-NOT transforms all Pauli products.

(c) Repeat parts (a) and (b) for the C-SIGN gate.

Notice that both C-NOT and C-SIGN take Pauli products to Pauli products.

(d) The circuit for superdense coding is shown below. The initial Hadamard–C-NOT combination creates the Bell entangled state $|\beta_{00}\rangle$. The first qubit is distributed to Alice, and the second is given to Bob. Alice encodes two bits, a and b , by applying $Z^a X^b$ to her qubit, yielding the Bell state $|\beta_{ab}\rangle$, and then sends her qubit to Bob. The C-NOT–Hadamard followed by measurement in the standard basis is equivalent to Bob’s measuring the two qubits in the Bell basis; thus Bob reads out the encoded data.

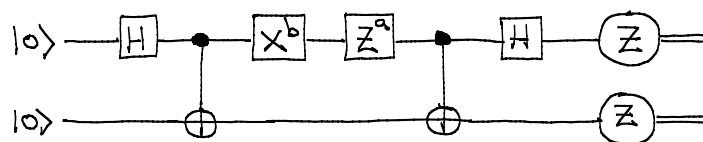

Use the transformation properties of the C-NOT to transform this circuit to an equivalent form for which it is obvious that the measurements yield a for the top qubit and b for the bottom qubit.