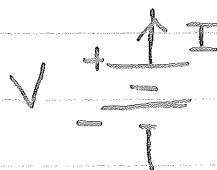


# Physics 406: Lecture 5: R, L, C Circuits

Inductors, capacitors, and resistors form the foundation of analog electronics. Let's review the fundamentals.


Circuit elements are defined by their I-V relations.

Voltage source (battery)



Current runs "uphill"

Ground

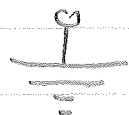

$$V = 0$$


Resistor



Current runs "downhill"

$$V_R = IR$$


Capacitor

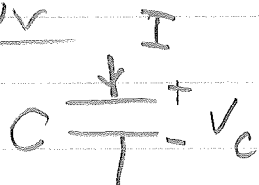

Current flows to charge up capacitor

$$I = C \frac{dV_C}{dt}$$

Inductor

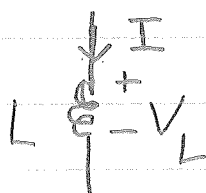

The "back EMF"  $\mathcal{E} = -V_L$

$$V_L = -\mathcal{E} = L \frac{dI}{dt}$$


(2)

## Kirchoff's Law (Quasistatics)

$$\sum_{\text{closed circuit}} V = 0 \quad \Leftrightarrow \oint \vec{E} \cdot d\vec{l} = 0$$

(when no flux through closed circuit)

R-L circuit

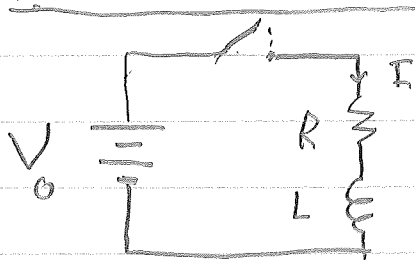


$$V_0 = V_R + V_L = IR + L \frac{dI}{dt}$$

$$\Rightarrow \frac{dI}{dt} = -\left(\frac{R}{L}\right)I + \frac{V_0}{L}$$

For short times ( $I$  small)  $\frac{dI}{dt} \approx \frac{V_0}{L} \Rightarrow I \approx \frac{V_0}{L} t$

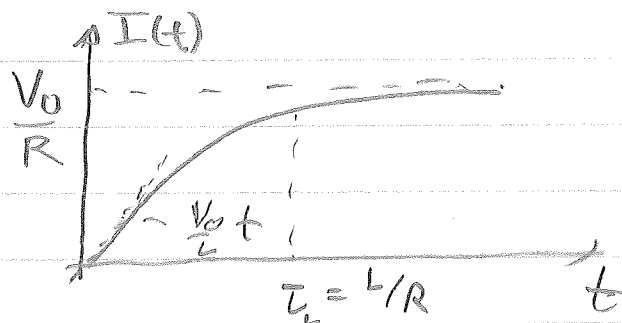For long times ( $\frac{dI}{dt}$  small)  $I \rightarrow \frac{V_0}{R}$



Full solution:  $I(t) = \underbrace{A e^{-\frac{R}{L}t}}_{\text{homogeneous solutio}} + \underbrace{\frac{V_0}{R}}_{\text{particular}}$

$$I(0) = 0 \Rightarrow A = -\frac{V_0}{R} \Rightarrow \boxed{I(t) = \frac{V_0}{R} (1 - e^{-\frac{R}{L}t})}$$


Inductors don't like changing current

- Acts as infinite resistor when  $\frac{dI}{dt}$  large
- Acts as "short circuit" for steady current

The "time constant" for steady state behavior

$$\tau_L = L/R$$

### R-C circuits

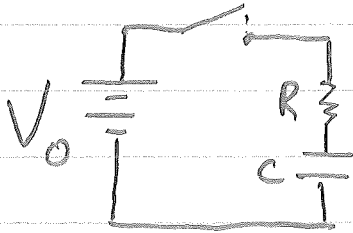

$$V_0 = V_R + V_C = IR + V_C$$


$$I = C \frac{dV_C}{dt}$$

$$\Rightarrow V_0 = RC \frac{dV_C}{dt} + V_C$$

$$\frac{dV_C}{dt} = -\frac{1}{RC} V_C + \frac{V_0}{RC}$$

Short time  
 $V_C = \frac{t}{RC} V_0$

Long time  
 $V_C = V_0$

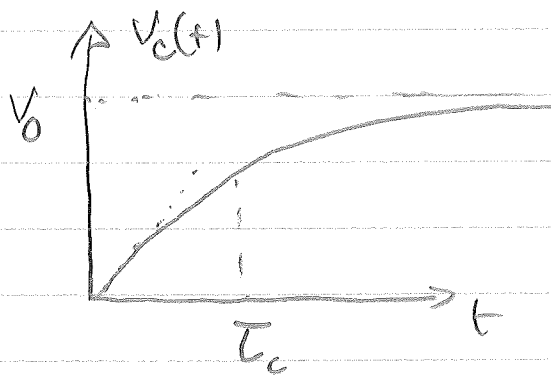

Full solution

$$V(t) = V_0 (1 - e^{-t/RC})$$

The time constant for charging the capacitor

$$\tau_c = 1/RC$$


Capacitors stop flowing current when voltage stops changing  $\Rightarrow$  Infinite resistor when  $\frac{dV}{dt}$  small.

## Alternating Current (AC)

Oscillating currents and voltage are central to physical phenomena and electronics.

Let's first establish the requisite mathematics.

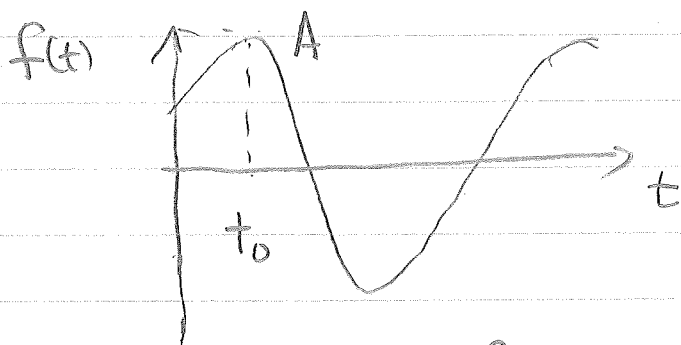Oscillating signal: period  $T$ , frequency  $\nu = \frac{1}{T}$   
 (cycles/sec)  
 $\uparrow$   
 Hertz



$$f(t) = A \cos\left(2\pi\left(\frac{t-t_0}{T}\right)\right)$$

$$= A \cos(\omega t - \phi_0)$$

$\uparrow$  Amplitude       $\uparrow$  phase

$$\omega = \frac{2\pi}{T} = \text{(angular freq)}$$

By trig:  $f(t) = \underbrace{A \cos \phi}_a \cos(\omega t) + \underbrace{A \sin \phi}_b \sin \omega t$

Any signal oscillating at (single) freq  $\omega$  is characterized by two numbers

$$\Rightarrow (\text{Amplitude: } A \quad \text{phase: } \phi_0)$$


$$\Rightarrow (\text{Quadratures: } \begin{matrix} \text{or} \\ a \text{ (amount of } \cos \omega t) \\ b \text{ (amount of } \sin \omega t) \end{matrix})$$

$$A = \sqrt{a^2 + b^2}, \quad \phi = \tan^{-1}(b/a)$$

Mathematically, instead of dealing with sine and cosine as separate functions, it is more convenient (and powerful) to employ the algebra of complex numbers based on Euler's formula

$$e^{-i\omega t} = \cos \omega t - i \sin \omega t \quad \left( \begin{array}{l} \text{minus sign is} \\ \text{a physics convention} \end{array} \right)$$

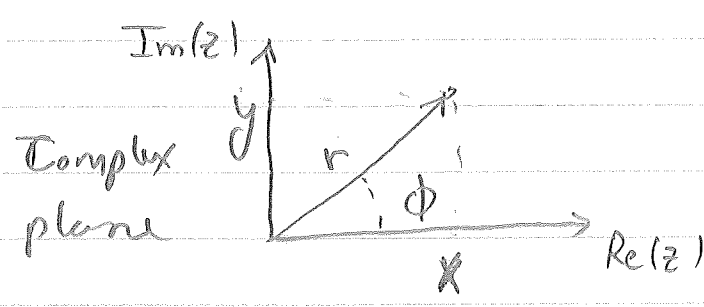Review of complex algebra  $i = \sqrt{-1}$



$$z = x + iy = r e^{i\phi}$$

$$x = \text{Re}(z) = r \cos \phi$$

$$y = \text{Im}(z) = r \sin \phi$$

$$r = |z| = \sqrt{x^2 + y^2}$$

$$\phi = \text{arg}(z) = \tan^{-1}\left(\frac{y}{x}\right)$$

• The real / imag decomposition useful for add/sub

$$z_1 \pm z_2 = (x_1 \pm x_2) \pm i (y_1 \pm y_2)$$

• The polar decomposition useful for mult/div (powers)


$$z_1^n z_2^m = r_1^n r_2^m e^{i(n\phi_1 + m\phi_2)}$$

• Important operation: Complex conjugate:  $z \rightarrow z^*$

$$z^* = x - iy = r e^{-i\phi}, \quad |z|^2 = z^* z = x^2 + y^2$$

6

## Application to AC Circuits

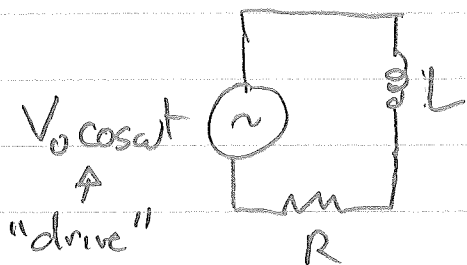

$$L \frac{dI}{dt} + IR = V_0 \cos \omega t$$

$$I(t) = I_{\text{homogeneous}} + I_{\text{particular}}$$

Homogeneous: Solution to  $\frac{dI}{dt} + \frac{R}{L} I = 0$

$$\Rightarrow I_{\text{homogeneous}} = I_0 e^{-R/Lt} \quad (\text{transient})$$

Particular: Solution when transients  $\Rightarrow 0$

Make ansatz  $I(t) = \text{Re}(\tilde{I} e^{-i\omega t})$

$$\tilde{I} = \text{"complex amplitude"} = |\tilde{I}| e^{i\phi_I}$$

The particular solution oscillates at freq of drive

$$\text{The drive: } V_D(t) = \text{Re}(V_0 e^{-i\omega t}) \quad (\text{reference phase} = 0)$$

Because the diff'eqn is linear we can look at both real and imaginary parts simultaneously and then take the real part in the end

$$L \frac{d(\tilde{I} e^{-i\omega t})}{dt} + (\tilde{I} e^{-i\omega t}) R = V_0 e^{-i\omega t}$$

"  $-i\omega \tilde{I} e^{-i\omega t}$  "

⇒ The diff' eqn becomes an algebraic eqn.

$$-i\omega \tilde{I}L + \tilde{I}R = V_0$$


$$\Rightarrow \tilde{I} = \frac{V_0}{R - i\omega L} = \frac{V_0}{\sqrt{R^2 + \omega^2 L^2}} e^{i\Delta\phi}$$

$$\Delta\phi = \tan^{-1}\left(\frac{\omega L}{R}\right)$$

⇒ Particular solution:


$$I_{\text{particular}} = \text{Re}\left(\tilde{I} e^{-i\omega t}\right) = \frac{V_0/R}{\sqrt{1 + \left(\frac{\omega L}{R}\right)^2}} \cos(\omega t - \Delta\phi)$$
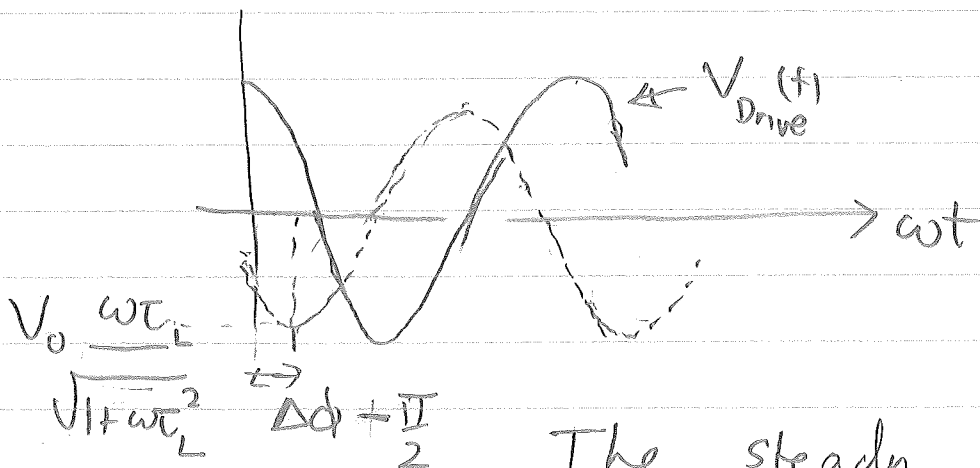
$$V_{\text{particular}} = L \frac{dI}{dt} = \left(\frac{-\omega L}{\sqrt{1 + \left(\frac{\omega L}{R}\right)^2}}\right) V_0 \sin(\omega t - \Delta\phi)$$



The steady state voltage across the inductor oscillates at the frequency of the drive. The signal is phase shifted due to finite response time.

(8)

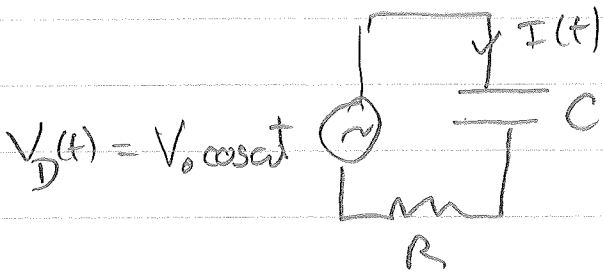AC-driven RC circuit

$$V_D(t) = V_C(t) + V_R(t)$$

$$\Rightarrow \frac{dV_D}{dt} = \frac{dV_C}{dt} + \frac{dV_R}{dt}$$

$$\Rightarrow \frac{d}{dt}(V_0 \cos \omega t) = \frac{I}{C} + \frac{dI}{dt} R$$

Steady state (Particular solution)

$$I(t) = \text{Re}(\tilde{I} e^{-i\omega t}), \quad V_D(t) = \text{Re}(V_0 e^{-i\omega t})$$

$$\Rightarrow -i\omega V_0 e^{-i\omega t} = \frac{\tilde{I}}{C} e^{-i\omega t} - i\omega \tilde{I} R e^{-i\omega t}$$

$$\Rightarrow \tilde{I} = \left( \frac{-i\omega}{-i\omega R + \frac{1}{C}} \right) V_0 = \frac{-i\omega RC}{1 - i\omega RC} V_0/R$$

$$\Rightarrow I(t) = \text{Re}(\tilde{I} e^{-i\omega t}) = \frac{V_0}{R} (\omega\tau_c) \text{Re} \left( \frac{-i e^{-i\omega t}}{1 - i\omega\tau_c} \right)$$

$\tau_c = RC$

$$\Rightarrow I(t) = \frac{V_0}{R} \frac{\omega\tau_c}{\sqrt{1 + (\omega\tau_c)^2}} \text{Re}(-i e^{-i(\omega t - \Delta\phi)})$$

$$\Delta\phi = \tan^{-1}(\omega\tau_c)$$

$$\Rightarrow I(t) = \frac{V_0}{R} \frac{\omega\tau_c}{\sqrt{1 + (\omega\tau_c)^2}} \sin(\omega t - \Delta\phi)$$



(9)


Thus the voltage drop across the capacitor

$$\frac{dV_c(t)}{dt} = \frac{I(t)}{C} \Rightarrow -i\omega \tilde{V}_c e^{-i\omega t} = \frac{\tilde{I} e^{-i\omega t}}{C}$$

$$\tilde{V}_c = \frac{\tilde{I}}{-i\omega C} = \left( \frac{1}{1-i\omega\tau_c} \right) V_0$$

$$\Rightarrow V_c(t) = \text{Re}(\tilde{V}_c e^{-i\omega t}) = \text{Re}\left(\frac{1}{1-i\omega\tau_c} V_0 e^{-i\omega t}\right)$$
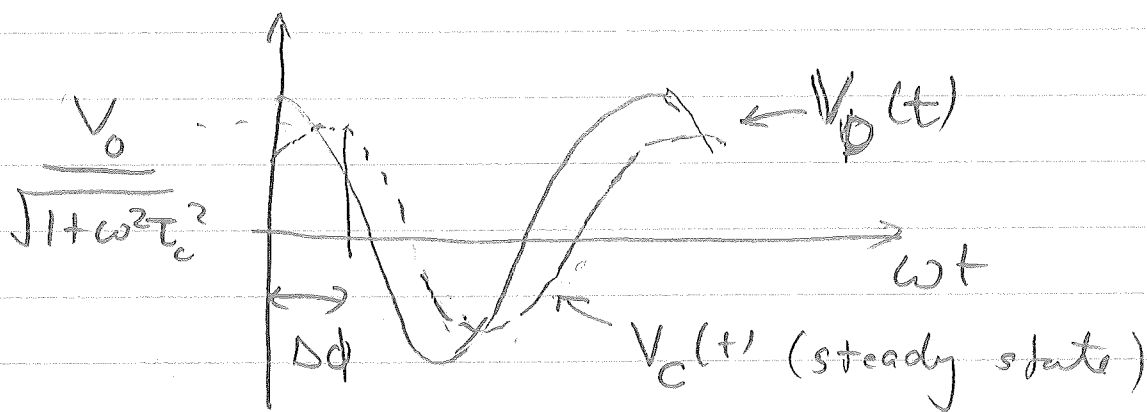
$$V_c(t) = \frac{V_0 \cos(\omega t - \Delta\phi)}{\sqrt{1+(\omega\tau_c)^2}}$$



Voltage across the capacitor

is also phase shifted in steady state