
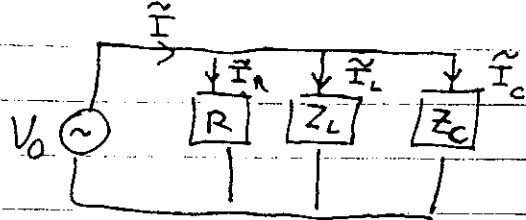


Physics 406

Problem Set #3 Solutions

Problem 1:

Parallel R-L-C circuit

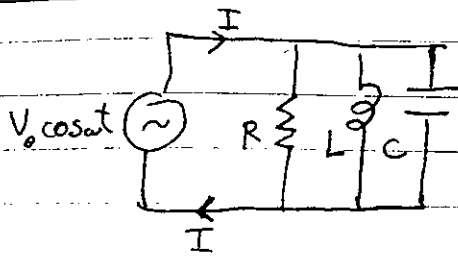

$$Z_R = R \quad Z_L = -i\omega L \quad Z_C = \frac{i}{\omega C}$$

Since the elements are in parallel

$$V_R = V_L = V_C = V_0$$

The total current divides between the elements

$$\tilde{I} = \tilde{I}_R + \tilde{I}_L + \tilde{I}_C = \tilde{V}/Z_R + \tilde{V}/Z_C + \tilde{V}/Z_L$$

$$\Rightarrow \tilde{I} = \left(\frac{1}{Z_R} + \frac{1}{Z_C} + \frac{1}{Z_L} \right) V_0 = \frac{V_0}{Z_{\text{total}}}$$

Parallel addition of impedances

$$\frac{1}{Z_{\text{total}}} = \frac{1}{Z_R} + \frac{1}{Z_C} + \frac{1}{Z_L} = \frac{1}{R} - i\omega C + \frac{i}{\omega L}$$

(a) On resonance $\omega = \frac{1}{\sqrt{LC}}$

$$\Rightarrow \frac{1}{Z_{\text{total}}} = \frac{1}{R} - i\sqrt{\frac{C}{L}} + i\sqrt{\frac{C}{L}} = \frac{1}{R}$$

$$\Rightarrow \tilde{I} = \frac{V_0}{R} \Rightarrow \boxed{I(t) = \text{Re}(\tilde{I} e^{-i\omega t}) = \frac{V_0}{R} \cos \omega t}$$

On resonance the magnitude of $|Z_L| = |Z_C| = \sqrt{\frac{L}{C}}$

but they are 180° out of phase so they cancel

On resonance a parallel L-C is like an open circuit.

(b) In general

$$I(t) = \operatorname{Re}(\tilde{I} e^{-i\omega t}) = \operatorname{Re}\left(\frac{V_0}{Z_{\text{total}}} e^{-i\omega t}\right)$$
$$= \frac{V_0}{|Z_{\text{total}}|} \cos(\omega t + \operatorname{Arg}(Z_{\text{total}}))$$

$$\frac{1}{|Z_{\text{total}}|} = \left| \frac{1}{Z_{\text{total}}} \right| = \left| \frac{1}{R} - i\left(\omega C - \frac{1}{\omega L}\right) \right|$$
$$= \sqrt{\frac{1}{R^2} + \left(\omega C - \frac{1}{\omega L}\right)^2} = \frac{1}{\omega L} \sqrt{\frac{\omega^2 L^2}{R^2} + (\omega^2 LC - 1)^2}$$
$$= \frac{1}{R} \frac{\Gamma}{\omega} \sqrt{\frac{\omega^2}{\Gamma^2} + \left(\frac{\omega^2}{\omega_0^2} - 1\right)}, \quad \Gamma = \frac{R}{L}$$
$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$\operatorname{Arg}(Z_{\text{total}}) = -\operatorname{Arg}\left(\frac{1}{Z}\right) = \tan^{-1}\left(\frac{\omega C - \frac{1}{\omega L}}{\frac{1}{R}}\right)$$
$$= \tan^{-1}\left(\frac{\Gamma}{\omega} \left(\frac{\omega^2}{\omega_0^2} - 1\right)\right)$$

$$\therefore I(t) = \frac{V_0}{R} \frac{\Gamma}{\omega} \sqrt{\frac{\omega^2}{\Gamma^2} + \left(\frac{\omega^2}{\omega_0^2} - 1\right)} \cos(\omega t + \operatorname{Arg}(Z_{\text{total}}))$$
$$\operatorname{Arg}(Z_T) = \tan^{-1}\left(\frac{\Gamma}{\omega} \left(\frac{\omega^2}{\omega_0^2} - 1\right)\right)$$

Note: On resonance, $I(t) = \frac{V_0}{R} \cos \omega t$
 $\operatorname{Arg}(Z_{\text{total}}) = 0$

Problem 2 Quality factor

(a) Math Lemma: Given $A(t) = A_0 \cos(\omega t - \phi_A)$
 $B(t) = B_0 \sin(\omega t - \phi_B)$

$$\text{Show } \langle A(t) B(t) \rangle = \frac{1}{T} \int_0^T dt A(t) B(t) = \frac{1}{2} \text{Re}(\tilde{A}^* \tilde{B}) \\ = \frac{1}{2} \text{Re}(\tilde{A} \tilde{B}^*)$$

$$\text{where } \tilde{A} = A_0 e^{i\phi_A} \quad A(t) = \text{Re}(\tilde{A} e^{-i\omega t}) \\ \tilde{B} = B_0 e^{i\phi_B} \quad B(t) = \text{Re}(\tilde{B} e^{-i\omega t})$$

Proof: There are lots of ways to do this, here's one of them

$$A(t) = \text{Re}(\tilde{A} e^{-i\omega t}) = \tilde{A}' \cos \omega t + \tilde{A}'' \sin \omega t \quad \left(\begin{array}{l} \text{where} \\ \tilde{A} = \tilde{A}' + i\tilde{A}'' \\ \tilde{B} = \tilde{B}' + i\tilde{B}'' \end{array} \right) \\ B(t) = \text{Re}(\tilde{B} e^{-i\omega t}) = \tilde{B}' \cos \omega t + \tilde{B}'' \sin \omega t$$

$$\therefore \langle A(t) B(t) \rangle = \tilde{A}' \tilde{B}' \langle \cos^2 \omega t \rangle + \tilde{A}'' \tilde{B}'' \langle \sin^2 \omega t \rangle \\ + (\tilde{A}' \tilde{B}'' + \tilde{A}'' \tilde{B}') \langle \cos \omega t \sin \omega t \rangle$$


$$\text{Now } \langle \cos^2 \omega t \rangle = \langle \sin^2 \omega t \rangle = \frac{1}{2} \quad \left. \begin{array}{l} \text{check} \\ \text{these} \end{array} \right\} \\ \langle \cos \omega t \sin \omega t \rangle = \frac{1}{2} \langle \sin 2\omega t \rangle = 0$$

$$\Rightarrow \langle A(t) B(t) \rangle = \frac{1}{2} (\tilde{A}' \tilde{B}' + \tilde{A}'' \tilde{B}'')$$

$$= \frac{1}{2} \text{Re}(\tilde{A} \tilde{B}^*) = \frac{1}{2} \text{Re}(\tilde{A}^* \tilde{B})$$

QED

(b) Power dissipated in an RLC circuit

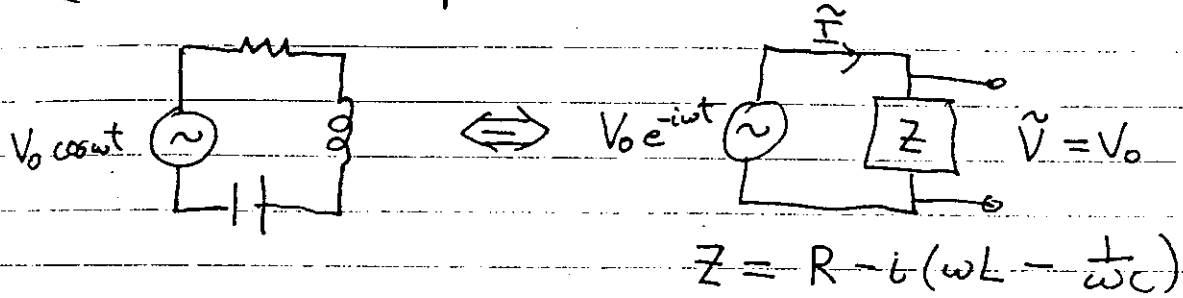

From part (a)

$$\langle P(t) \rangle = \langle V(t) I(t) \rangle = \frac{1}{2} \text{Re}(\tilde{V} \tilde{I}^*)$$

Here \tilde{V} and \tilde{I} are the complex amplitudes of the voltage and current across the load

$$\tilde{V} = V_0 \quad \tilde{I} = \frac{\tilde{V}}{Z} = \frac{V_0}{Z}$$

$$\therefore \langle P \rangle = \frac{1}{2} \text{Re} \left(\frac{V_0^2}{Z} \right) = \frac{V_0^2}{2} \text{Re} \left(\frac{1}{R - i(\omega L - \frac{1}{\omega C})} \right)$$

$$= \frac{V_0^2}{2} \text{Re} \left(\frac{R + i(\omega L - \frac{1}{\omega C})}{R^2 + (\omega L - \frac{1}{\omega C})^2} \right) \quad \begin{array}{l} \text{Multiplying top and bottom} \\ \text{by } R + i(\omega L - \frac{1}{\omega C}) \end{array}$$

$$= \frac{V_0^2}{2} \frac{R}{R^2 + (\omega L - \frac{1}{\omega C})^2}$$

$$= \frac{V_0^2}{2R} \frac{\frac{R^2}{L^2} \omega^2}{\omega^2 \frac{R^2}{L^2} + (\omega^2 - \frac{1}{LC})^2} \quad \left(\begin{array}{l} \text{multiplying} \\ \text{top and bottom} \\ \text{by } \frac{\omega^2}{L^2} \end{array} \right)$$

$$= \frac{V_0^2}{2R} \frac{\Gamma^2 \omega^2}{\omega^2 \Gamma^2 + (\omega^2 - \omega_0^2)^2}$$

where $\Gamma \equiv \frac{R}{L} \quad \omega_0 = \frac{1}{LC}$


Now in the near resonance approximation

$$\omega^2 - \omega_0^2 = (\omega - \omega_0)(\omega + \omega_0) \approx 2\omega(\omega - \omega_0)$$

$$\Rightarrow \langle P \rangle = \frac{V_0^2}{2R} \frac{\Gamma^2 \omega^2}{\omega^2 \Gamma^2 + 4\omega^2(\omega - \omega_0)^2}$$

$$\langle P \rangle = \frac{V_0^2}{2R} \frac{\Gamma^2/4}{(\omega - \omega_0)^2 + \frac{\Gamma^2}{4}}$$

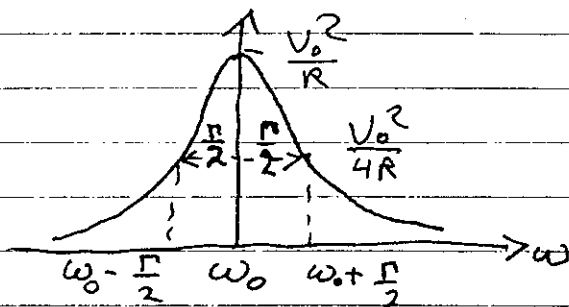Near the resonance, the $\langle \text{Power} \rangle$ dissipated looks like a Lorentzian



$$\text{FWHM} = \Gamma$$

(c) The average stored energy is the sum of energies in C +

$$\langle E \rangle = \langle E_C \rangle + \langle E_L \rangle = \frac{1}{2} \langle V_C^2 \rangle + \frac{1}{2} L \langle I_L^2 \rangle$$

But $\langle E_C \rangle = \langle E_L \rangle$ (capacitor + inductor store equal energies)

$$\Rightarrow \langle E \rangle = 2 \langle E_L \rangle = L \langle I_L^2 \rangle$$

$$= L \left(\frac{\text{Re} \langle \tilde{I} \tilde{I}^* \rangle}{2} \right) = \frac{L}{2} \text{Re} \left(\frac{\tilde{V}}{Z} \frac{\tilde{V}^*}{Z^*} \right)$$

$$= \frac{L}{2} \frac{V_0^2}{|Z|^2}$$

On resonance $Z = R \Rightarrow \langle E(\omega = \omega_0) \rangle = \frac{L V_0^2}{2 R^2}$

On resonance, the average power dissipated is


$$\langle P \rangle |_{\omega=\omega_0} = \frac{V_0^2}{2R}$$

$$\therefore Q \equiv \omega_0 \frac{\langle E \rangle}{\langle P \rangle} = \omega_0 \frac{\frac{L V_0^2}{2R^2}}{\frac{V_0^2}{2R}}$$


$$\Rightarrow \boxed{Q = \omega_0 \frac{L}{R} = \frac{\omega_0}{\Gamma}}$$

This is the general form of Q : ratio of oscillation frequency to the damping rate.

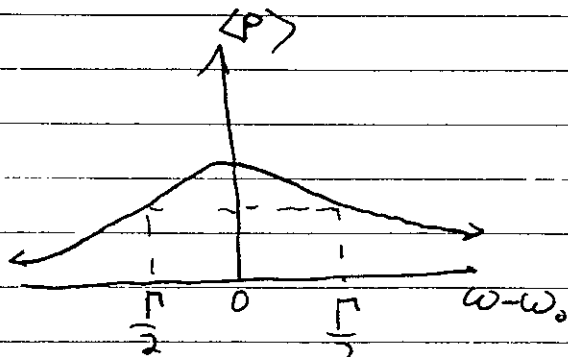It measures the number of periods oscillated before the stored energy decays to $1/e$ of its value. For a good oscillator Q is very large ($\sim 10^4$). The resonance is then very narrow (i.e. if we want to deliver power to the load we must be almost exactly on resonance);




Low Q
(R big)

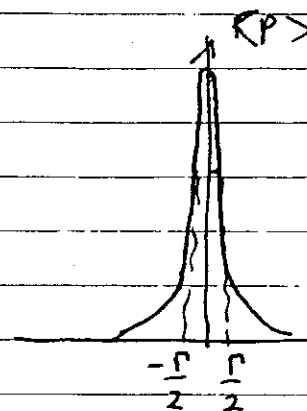

High Q
(R small)

Problem 3 Griffiths 7.16

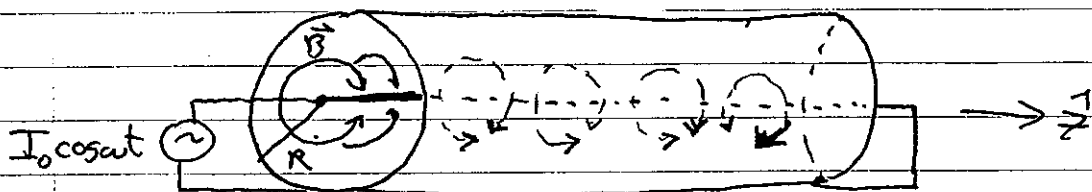


7.16 (a) The magnetic field lines point in the azimuthal direction (alternating from $+\hat{\phi}$ to $-\hat{\phi}$)

Remember that Faraday's Law for \vec{E} is like Ampere's Law for \vec{B} with magnetic flux playing the role of current density:

$$\begin{aligned} \vec{\nabla} \times \vec{E} &= -\frac{\partial \vec{B}}{\partial t} \\ \Downarrow & \quad \Downarrow \\ \vec{\nabla} \times \vec{B} &= \mu_0 \vec{J} \end{aligned}$$

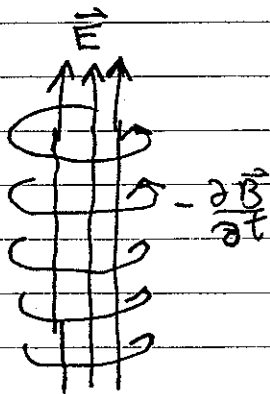The magnetic flux lines are changing in the $\hat{\phi}$ direction. This is like current going in the $\hat{\phi}$ direction i.e. a SOLENOID! Thus, \vec{E} points in the \hat{z} direction




Also from symmetry the magnitude of \vec{E} depends only on the distance from the axis r

$$\Rightarrow \boxed{\vec{E} = E(r) \hat{z}}$$

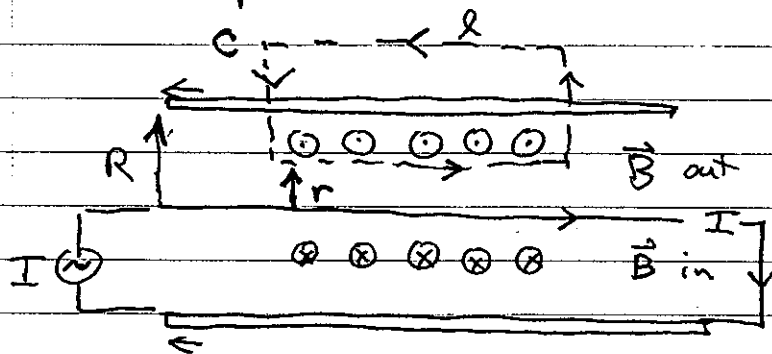7.16 (b) Look at the coaxial cable in cross-section.

• For an effectively infinite cylinder, \vec{E} is zero outside $r > R$ as for a solenoid.

• The \vec{B} field is zero for $r > R$ from Ampere's Law



At some instant of time the field will be in such a configuration

Now take Faraday's Law around contour C

$$\oint_C \vec{E} \cdot d\vec{l} = \underbrace{E(r)l}_{\text{bottom leg}} + \underbrace{0 + 0 + 0}_{\substack{\text{side legs} = 0 \\ \text{because } \vec{E} \perp d\vec{l}}} + \underbrace{0}_{\substack{\text{top leg} = 0 \\ \text{because } |\vec{E}| = 0 \\ \text{for } r > R}}$$

$$\begin{aligned} \Phi_B &= \int_S \vec{B} \cdot d\vec{a} = l \int_r^R dr' B(r') = l \int_r^R dr' \frac{\mu_0 I(t)}{2\pi r'} \\ &= l \frac{\mu_0 I(t)}{2\pi} \ln\left(\frac{R}{r}\right) = l \frac{\mu_0 I_0 \cos \omega t}{2\pi} \ln\left(\frac{R}{r}\right) \end{aligned}$$

$$\therefore -\frac{d\Phi_B}{dt} = +l \frac{\mu_0 \omega I_0 \sin \omega t}{2\pi} \ln\left(\frac{R}{r}\right)$$

$$\Rightarrow \boxed{\vec{E}(r) = \frac{\mu_0 \omega I_0}{2\pi} \sin \omega t \ln\left(\frac{R}{r}\right) \hat{z}}$$